## **GUJARAT TECHNOLOGICAL UNIVERSITY** PDDC- SEMESTER VII- • EXAMINATION – SUMMER - 2016

	•		Date:25/11/2016	
Subject Name: Power ElectronicsTotalTime: 10:30 AM to 1:00 PMTotalInstructions:1. Attempt all questions.2. Make suitable assumptions wherever necessary.3. Figures to the right indicate full marks.		0:30 AM to 1:00 PM Total Marks: ons: Attempt all questions. Make suitable assumptions wherever necessary.	Marks: 70	
Q.1	<b>(a)</b>	Explain the operation of the SCR using the two transistor analogy. Obtain the condition for breakdown of the device.	07	
	<b>(b)</b>	Classify commutation techniques. Discuss class-C Commutation circuit for SCR.	07	
Q.2	<b>(a)</b>	Describe the construction & working of IGBT. Also enumerate the advantage of IGBT over BJT & MOSFET.	07	
	(b)	Explain the phase control SCR using UJT with necessary waveforms. OR	07	
	<b>(b)</b>	Briefly explain the series operation of SCR with necessary equations.	07	
Q.3	(a) (b)	Classify the chopper. List all types of chopper and explain any two in detail. Draw and explain single phase full converter with inductive load using necessary waveforms and equation.	07 07	
Q.3	(a)	<b>OR</b> Explain di/dt and dv/dt protection for thyristor.	07	
Q.3	(a) (b)	Explain three-phase half-wave controlled rectifier with resistive load.	07 07	
Q.4	(a) (b)	Describe three-phase bridge inverter with $180^0$ mode of conduction. Explain working principle of Buck regulator with the help of circuit diagram and waveforms.	07 07	
Q.4	(a)	<b>OR</b> Explain single phase full bridge inverter with necessary waveforms.	07	
Q.4		Discuss the principle of step down chopper with suitable waveforms.	07 07	
Q.5	(a) (b)	Describe Switched Mode Power Supply with necessary diagram in detail. List types of heating mechanism available and Explain any one in detail. <b>OR</b>	07 07	
Q.5	(a) (b)	Describe UPS with necessary diagram in detail. Explain battery charger with necessary diagram.	07 07	
		****		

\*\*\*\*\*