GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER – II • EXAMINATION – WINTER 2012

Subject code: X 20902 Date: 24/01/20			13
•		me: Electrical Measurement I & II 0 am - 01.00 pm Total Marks:	70
	uctio	-	
	1. At	tempt all questions.	
		ake suitable assumptions wherever necessary. gures to the right indicate full marks.	
	51 118		
Q.1	(a)	Define following terms (i) Sensitivity (ii) Precision (iii) Hysteresis (iv) Drift	07
	(b)	With neat sketch explain the two-wattmeter method of power measurement.	07
Q.2	(a)	Explain working principle of megger.	07
	(b)	Explain various effects with which deflecting torque is produced? OR	07
	(b)	Explain difference between Gravity control and spring control.	07
Q.3	(a)	Which are the different methods of power measurement in 1-ph and 3-ph systems.	07
	(b)	State the different methods of measuring medium resistances. Explain any one method in brief.	07
		OR	
Q.3	(a)	Explain how the current range of a PMMC instrument can be extended? Also derive equation for shunt.	07
	(b)	Explain the construction and working principle of Dynamometer type instruments.	07
Q.4	(a)	Draw the circuit diagram of Schering bridge and derive expression for C and tan δ at balance for dielectric under test.	07
	(b)	With phase diagram explain the working principle of current transformer, State its applications. OR	07
Q.4	(a)	What is the importance of Wien's bridge? Explain in brief.	07
Q.4	(b)	Draw the circuit diagram of Anderson's bridge. State the application of the bridge.	07
Q.5	(a)	Discuss with neat diagram the DC potentiometer-Crompton potentiometer with its calibration and test procedure.	14
		OR	
Q.5	(a) (b)	Discuss the different methods of damping in indicating instruments. Construction and working of D'Arsonval galvanometer.	07 07

ig of D Afsonval g