Enrolment No.

## GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER - III • EXAMINATION - WINTER 2012

Date: 26/12/2012 Subject code: X 30901 **Subject Name: Basic Electronics** Time: 10.30 am - 01.00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 0.1 (a) Explain forward and reverse characteristics of PN junction diode. Also explain its 07 current components during forward and reverse bias. Explain construction and working of PNP & NPN transistor. 07 (a) Explain full wave rectifier with centre tape and derive its output equation. 0.2 07 **(b)** Explain shunt clipper circuit with bias and no bias. 07 Explain diode ideal and real characteristics with equivalent circuit. **(b) 07** 0.3 (a) Give the comparison between different transistor configurations. 07 Explain about photo diode and photo transistor. **(b)** 07 OR (a) Explain half wave rectifier circuit with inductive and capacitive filter. 0.3 07 **(b)** Explain series and shunt clamper circuit using diode. 07 (a) Give the comparison between half-wave rectifier, full-wave rectifier with centre tape and 0.4 07 full-wave bridge rectifier. (b) Explain the input and output characteristics of CB configuration of transistor. 07 0.4 Why the stability of operating point is necessary when transistor is used as amplifier. (a) 07 Explain the hybrid model for CE configuration of transistor and obtain its parameter. **Q.4 (b)** 07 0.5 (a) Explain class A and class B amplifier using transistor. 07 **(b)** Explain transistorized push-pull amplifier. 07 Explain construction of JFET and define its all parameters. Q.5 07

\*\*\*\*\*

stability.

(b) Explain different bias compensation techniques used for transistor operating point

07