Seat No.:

Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER – VII • EXAMINATION – WINTER 2012

Subject code: X 70904 Subject Name: Advanced Power System - I	Date: 01/01/2013
Time: 10.30 am - 01.00 pm Instructions:	Total Marks: 70
 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. Q.1 (A) Explain working of STATCOM with schematic diagram. 	[7]
Q.1 (B) Explain schematic diagram of HVDC substation and explain in brief.Q.2 (A) Comparison between the classical HVDC and HVDC-VSC	[7]
Q.2 (B) Explain working of TCR draw wave forms of voltage and α .	current for different values of [7]
OR	
Q.2 (B) Explain extinction angle control? What are its limitations un	der asymmetrical fault? [7]
Q.3 (A) State difference in power control in HVDC and HVAC syst	em. [7]
Q.3 (B) Identify the various sources for generation of harmonics various adverse effects caused due to the presence of harmonics.	s in HVDC system. Discuss [7]
OR	
Q.3 (A) Explain different methods of Reactive power control.	[7]
Q.3 (B) Discuss in brief various sources and sinks of reactive power	in power system. [7]
Q.4 (A) Explain modeling of thyristor controlled reactor (TCR expressions and usual notations.Q.4 (B) What are the different types of HVDC links? Explain any or	[7]
OR	
Q.4 (A) Explain conduction sequence in 6-pulse converter configuration used for HVDC system.	
[7] Q.4 (B) Sketch the current waveform of the transformer secondar converter. Derive expressions for PIV and PPR for 12 pulse converter	
Q.5 (A) Explain load compensation and system compensation with the help of phasor diagram.	
[7] Q.5 (B) What is meant by compensation? Discuss shunt and se system.	ries compensation in power [7]
OR Q.5 (A) Sketch and explain characteristics of an ideal & realistic Static VAR System (SVS). [7]	
Q.5 (B) Discuss advantages of FACTS.	[7] [7]
