

GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-II • EXAMINATION – WINTER 2013

Subject Code: X20902**Date: 23-12-2013****Subject Name: Electrical Measurement I & II****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Derive the dimensions of a) e.m.f., b) magnetic flux density, c) electric flux density, d) current density, e) permeability, f) permittivity, g) resistivity in L,M,T,I system of dimensions. 7
- (b) Explain construction and working of PMMC instruments. 7
- Q.2** (a) Describe the constructional details and working of the electro-dynamometer type instrument. How dynamometer type instrument is used as an ammeter, voltmeter and wattmeter? 7
- (b) Explain construction and working of DArsonval Galvanometer with neat sketch. 7
- OR**
- (b) Show that in two wattmeter method of power measurement for 3- ϕ balanced load system, the total power consumed is the sum of reading of two watt meters. 7
- Q.3** (a) Explain working principle of Slide wire D.C. potentiometer. Also explain how it is standardized. 7
- (b) Derive the torque equation for induction type single phase energy meter. 7
- OR**
- Q.3** (a) Explain Maxwell's inductance capacitance bridge with connection diagram and phasor diagram also state balance condition for the same. 7
- (b) Describe working of low voltage Schering bridge. Derive equation of capacitance and dissipation factor 7
- Q.4** (a) Describe Wein's Bridge and derive the expression of frequency in terms of its parameters. 7
- (b) Draw the circuit of Kelvin's double bridge used for measurement of low resistance. Derive the condition for balance. 7
- OR**
- Q.4** (a) State the methods for measurement of high resistance and Explain the construction and working of meggar. 7
- (b) Describe De Sauty's Bridge and derive the equation for the same. 7
- Q.5** (a) Draw the equivalent circuit and phasor diagram of a current transformer. Derive the expression for ratio and phase angle errors. 7
- (b) Draw the circuit of a Wheatstone bridge and derive the condition of balance. 7
- OR**
- Q.5** (a) Draw the circuit diagram of a Crompton's potentiometer and explain its working. 7
- (b) Describe the construction and operation of 1- ϕ induction type energy meter. 7
