

GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-IV • EXAMINATION – WINTER 2013

Subject Code: X41103**Date: 07-12-2013****Subject Name: Integrated Circuits and Applications****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Derive the equations of gain, input resistance, output resistance, bandwidth and total output offset voltage with feedback for voltage series feedback amplifier. **07**
- (b) Draw and explain basic block diagram of op-amp and list out ideal characteristics of op-amp **07**
- Q.2** (a) The 741c op-amp having following parameters is connected as a noninverting amplifier with $R_1 = 1.5\text{kohm}$ and $R_F = 15\text{kohm}$: $A = 200000$, $R_i = 2\text{Mohm}$, $R_o = 75\text{ohm}$, $f_o = 5\text{Hz}$, supply voltage = $\pm 15\text{V}$, output voltage swing = $\pm 13\text{V}$. Compute the values of A_F , R_{iF} , R_{oF} , f_F , and V_{ooT} **07**
- (b) Explain summing, scaling and averaging amplifier in detail **07**
- OR**
- (b) Explain instrumentation amplifier in brief and derive equation of output voltage for instrumentation amplifier using transducer bridge **07**
- Q.3** (a) Explain differential input and differential output amplifier in detail **07**
- (b) Explain integrator in detail **07**
- OR**
- Q.3** (a) Explain square wave generator using op-amp in detail **07**
- (b) Explain differentiator in detail **07**
- Q.4** (a) Explain schmitt trigger in detail **07**
- (b) Explain absolute-value output circuit in detail **07**
- OR**
- Q.4** (a) Explain peak clamper circuit in detail **07**
- (b) Explain sample-and-hold circuit in detail **07**
- Q.5** (a) Explain 555 timer as a monostable multivibrator in detail **07**
- (b) Explain phase-locked loop with block diagram and operating principle **07**
- OR**
- Q.5** (a) Explain biquad circuit in detail. Also explain orthogonally tuned property of the biquad circuit **07**
- (b) Design a bandpass filter with a center frequency at $\omega_o = 1000\text{ rad/s}$, a bandwidth of 200 rad/s , and maximum gain of 1, using the biquad circuit. **07**
