

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-V • EXAMINATION – WINTER 2013

Subject Code: X 50903

Date: 09-12-2013

Subject Name: Power Electronics-II

Time: 10.30 am - 01.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the working of Mac- Murray Bedford inverter circuit with waveforms, Describe each interval of operation. 7
- (b) Draw and explain the series Inverter circuit employing Class-A type commutation. Draw and discuss the important waveforms. 7

- Q.2** (a) List various PWM methods used in inverters for Harmonic reduction and explain Sinusoidal Pulse Modulation with necessary waveforms. 7
- (b) Give the comparison between On/Off control and phase control of A.C voltage controller. 7

OR

- (b) Discuss the operation of single phase A.C voltage regulator with R-L load, when α is less than or equal to load phase angle ϕ . Hence show that for α less than the output voltage of A.C voltage regulator cannot be regulated. 7
- Q.3** (a) State the various points of comparisons and their choice/criterion for selection between AC and DC drives. 7
- (b) Explain the principle of operation of three phase bridge inverter with 180 ° conduction mode with necessary circuit diagram and waveforms. 7

OR

- Q.3** (a) Draw the neat circuit diagram of three phase full wave bidirectional AC Voltage controller and explain it's working with waveforms for different firing angles. 7
- (b) Name the different methods of speed control of 3- ϕ Induction motor. Explain the principle of speed control of it by PWM method 7

- Q.4** (a) Describe using a neat circuit diagram, waveform and operation of PWM inverter and also explain how the output voltage can be controlled in this scheme. 7
- (b) Describe the basic principle of single phase to single phase cycloconverter for both Continuous and discontinuous conduction for bridge type cycloconverter. 7

OR

- Q.4** (a) Draw the circuit diagram and explain the working of slip power recovery system using solid state scherbius system. 7
- (b) Draw the torque speed characteristics of 3 phase Induction motor and explain the following regions. (1).Plugging (2).Motoring 7

- Q.5** (a) Differentiate voltage source inverter with current source inverter. 7
- (b) Draw the neat circuit diagram and explain the speed control of 3 ϕ Induction motor by rotor resistance control method using chopper. 7

OR

- Q.5** (a) Draw and explain the operation of DC static circuit breaker and list it's applications. 7
- (b) Explain the stator voltage control of induction motor drives. 7
