GUJARAT TECHNOLOGICAL UNIVERSITY

Date: 01-01-2015

PDDC - SEMESTER-I • EXAMINATION – WINTER • 2014

Subject Code: X11101

	-	Name: Basic Electronics 0:30 am - 01:00 pm Total Marks: 70	
Instr	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain the formation of potential barrier in a PN junction. Why silicon is preferred to germanium in the manufacturing of semiconductor devices? Explain the concept of potential energy barrier.	07 07
Q.2	(a) (b)	Define the term rectification and describe the full wave bridge rectifier with the help of neat circuit diagram and waveforms. Explain construction and working of Tunnel diode. OR	07 07
Q.3	(b) (a) (b)	State and explain Miller's theorem and its duality. Explain the principle of operation of photodiode. List its applications. Explain CC configuration of transistor with its input and output Characteristics.	07 07 07
Q.3	(a) (b)	Give the differences between clipper and clamper. And explain the positive clipping and negative clamper circuit. A transistor with $\beta=100$ is to be used in common emitter configuration with collector to base bias. The collector circuit resistance is $R_C=1k\Omega$ and $V_{CC}=10$ V. Assume $V_{BE}=0$, Choose R_B so that the quiescent collector to emitter voltage is 4 V. also find the stability factor.	07 07
Q.4	(a) (b)	What is the need of biasing in case of transistor? List different biasing method and explain any one. Explain the output characteristic of NPN transistor in CE configuration also indicate the different region.	07 07
Q.4	(a) (b)	Explain the h-parameter model of CE amplifier with bypass resistance R_E and derive expression for A_i , A_v , R_i and R_o . Define the term voltage gain, current gain and power gain for the transistor. If a transistor have value of $\alpha = 0.96$ and emitter to base resistance $80~\Omega$ is placed in common emitter configuration. Determine A_I , A_V and A_P .	07 07
Q.5	(a) (b)	Write a brief note on Thermal Runaway and Thermal Stability. Explain the principle of operation of JFET. Also compare FET with BJT. OR	07 07
Q.5	(a) (b)	Classify the power amplifiers based on the position of Q-point on the ac load line. Also explain Class B push pull amplifier. Explain the cross section of N channel enhancement MOSFET with the help of neat sketch. Draw and explain the symbol of this device.	07 07
