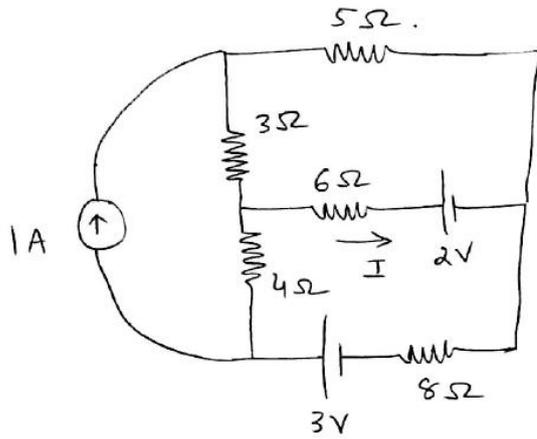


GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-II • EXAMINATION – WINTER • 2014


Subject Code: X20901**Date: 26-12-2014****Subject Name: Circuits and Networks****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.


- Q.1** (a) State and explain maximum power transfer theorem. **07**
 (b) Discuss duality between Thevinin's and Norton's theorem. **07**
- Q.2** (a) Determine current 'I' using source transformation techniques in fig. 1. **07**
 (b) Determine Impedance parameter set for the network shown in fig. 2. **07**
- OR**
- (b) Determine transmission line parameter set for the network shown in fig. 2. **07**
- Q.3** (a) Determine current through 2 ohm resistor in fig. 3 using mesh analysis. **07**
 (b) Explain significance of dot in magnetically coupled circuits. **07**
- OR**
- Q.3** (a) Determine current through 2 ohm resistor in fig. 3 using Node voltage analysis. **07**
 (b) Discuss application of Laplace transformation in circuit analysis. Give suitable example. **07**
- Q.4** (a) Explain dependant current and voltage sources with suitable example. **07**
 (b) In the circuit shown in fig. 4 switch k is opened at t=0. Determine v, dv/dt and d^2v/dt^2 at t=0+. **07**
- OR**
- Q.4** (a) Discuss concept of complex frequency. **07**
 (b) Prepare graph tree and co tree for the network shown in fig. 5 **07**
- Q.5** (a) Explain cascade connection of two port network. **07**
 (b) Explain various source transformation techniques. **07**
- OR**
- Q.5** (a) Explain how any two port network can be represented by simplified 'T' or 'π' network using two port parameter sets. **07**
 (b) Use superposition theorem to find current through 10 V source in fig -3. **07**




(Fig-1).

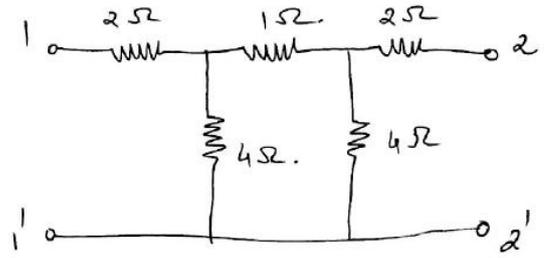


(Fig-2).

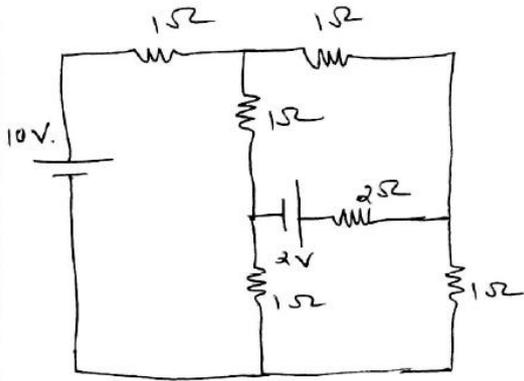

(Fig-3).

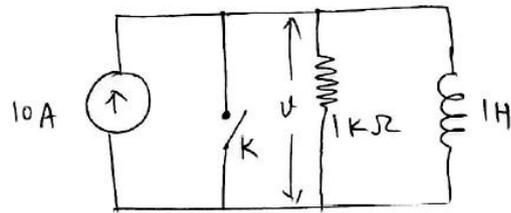

(Fig-4).

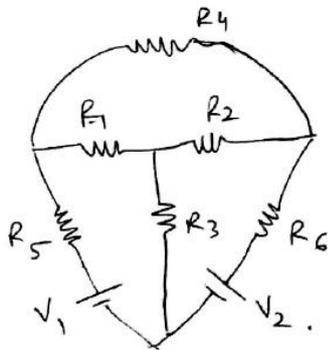

(Fig-5).