	Sea	t No.: Enrolment No	
		GUJARAT TECHNOLOGICAL UNIVERSITY	
		PDDC - SEMESTER-II • EXAMINATION – WINTER • 2014	
	Su	bject Code: X20902 Date: 30-12-2014	
		bject Name: Electrical Measurement I and II	
		ne: 02:30 pm - 05:00 pm Total Marks: 70	
		tructions:	
		 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 	
Q.1	(a) (b)	Explain construction and working of Maxwell bridge. Construction and working of D'Arsonval galvanometer.	7 7
Q.2	(a)	Define and explain: 1. True value, 2. Precision, 3. Error, 4. Sensitivity, 5. Resolution, 6. Accuracy. 7. Threshold.	7
	(b)	Define Gauge factor with respect to resistance strain gauge. Obtain an expression for the gauge factor in terms of poison's ratio.	7
		OR	
	(b)	Explain with suitable diagram de'sauty's bridge	7
Q.3	(a)	Explain Drysdale-Tinsley polar type AC potentiometer Describe the constructional details and working of the electrodynamometer type instrument	7 7
	(b)	Describe the constructional details and working of the electrodynamometer type instrument. How	,
		dynamometer type instrument is used as an ammeter, voltmeter and wattmeter?	
0.0	()	OR	_
Q.3	(a)	Show that in two wattmeter method of power measurement for 3-Ø balanced load system, the total power consumed is the sum of reading of two watt meters.	7
	(b)	Explain working principle of Slide wire D.C. potentiometer. Also explain how it is standardized.	7
Q.4	(a)	Derive the torque equation for induction type single phase energy meter	7
	(b)	What do you understand by Low, Medium and High resistance? Describe Kelvin's double bridge method for measurement of small resistance.	7
		OR	
Q.4	(a)	Describe the Construction and working of a Single phase energy meter	7
	(b)	Explain construction and working of Anderson bridge.	7
Q.5	(a)	Construction and working of resonance type frequency meter	7
	(b)	Explain construction and working of Mexwell bridge	7
~ -		OR	_
Q.5	(a)	Explain construction and working of a basic electronic voltmeter	7
	(b)	With suitable vector diagram explain working principal of a potential transformer. Define ratio	7
		and phase angle errors. Discuss applications of a P.T ***********************************	