

GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-IV • EXAMINATION – WINTER • 2014

Subject Code: X41103**Date: 31-12-2014****Subject Name: Integrated Circuits and Applications****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain application of Op-amp (Non Inverting Configuration) as Summing, Scaling and averaging circuit. **07**
- (b) Draw block diagram of a typical op-amp and explain functions of each block. **07**

- Q.2** (a) Explain various types of open loop configuration. **07**
- (b) Define following terms 1.CMRR 2.PSRR 3.Slew Rate 4.Input Offset voltage 5.Input Offset current 6.Input bias current 7.Equivalent input noise voltage and current **07**

OR

- (b) Draw the high frequency model of an Op-Amp and Obtain the expression for the open loop gain as a function of frequency. **07**

- Q.3** (a) What do you mean by precision rectifier? Explain with necessary diagram the working of precision full wave rectifier by using Op-amp. **07**
- (b) Draw the Schmitt trigger comparator circuit and explain threshold levels and hysteresis. **07**

OR

- Q.3** (a) Draw and explain log as well as antilog amplifier circuit by using Op-amp. **07**
- (b) Draw and explain voltage limiters circuits by Op-amp. **07**

- Q.4** (a) Design a differentiator circuit by using Op-amp to differentiate an input signal that varies in frequency from 10 Hz to about 1 KHz. **07**
- (b) With the help of a circuit diagram explain the operation of first order active high pass filter and draw its frequency response characteristics. **07**

OR

- Q.4** (a) Draw and explain the circuit diagram of voltage to current converter with grounded as well as floating load. **07**
- Q.4** (b) Derive the expression for filter transfer function of first order active low-pass filter and draw its frequency response characteristics. **07**

- Q.5** (a) Draw and explain square wave generator by using Op-amp. **07**
- (b) Explain with a neat circuit diagram and waveforms, the operation of monostable multivibrator using 555 timer. **07**

OR

- Q.5** (a) Draw block diagram of the PLL system and explain function of each block. State the applications of PLL. **07**
- (b) Draw and explain the block diagram of 555 timer IC as well as explain the function of each pin of 555 timer IC. **07**
