GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-VIII • EXAMINATION – WINTER • 2014

	0	Code: X80905 Date: 03-12-2014	
Ti	me:02 tructio 1. 2.	Attempt all questions.	
Q.1	(a) (b)	State and explain advantages and limitations of FACTs. Write a short note on automatic generation control with necessary diagrams.	07 07
Q.2	(a) (b)	Write a short note on phase shifting transformer with necessary diagrams. Compare series and shunt compensation for transmission lines. OR	07 07
	(b)	Write a short note on effect of compensation on power transfer capacity.	07
Q.3	(a) (b)	Write a short note on working of TCT with suitable diagrams. Explain working principles of TCR with necessary diagrams. OR	07 07
Q.3	(a) (b)	Write a short note on FC-TCR with necessary diagrams. Explain working principles of TSCTCR with suitable digrams.	07 07
Q.4	(a) (b)	Write a short note on HVDC-VSC Principles and Operation with suitable diagrams. Explain three phase six pulse converter using SCRs with necessary sketches.	07 07
	(0)	OR	07
Q.4	(a)	Discuss following in relation to HVDC link:	07
	(b)	1.Power flow in HVDC link. 2. Conduction sequence in Six Pulse Converter. Write a short not on twelve pulse bridge converters.	07
Q.5	(a) (b)	Discuss Inverter Extinction Angle Control (EAG) in details. Draw and explain each block diagram of HVDC substation. OR	07 07
Q.5	(a) (b)	Compare HVDC transmission line to HVAC transmission lines. Explain power reversal in DC link in HVDC transmission lines.	07 07
