Seat No.:		Seat No.: Enrolment No	
	В	GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER- 1 st / 2 nd EXAMINATION (NEW SYLLABUS) - SUMMER 2015	
Subj	ect (Code: 2110016 Date: 09/06/201	5
Subj	ect N	Name: BASIC ELECTRONICS	
Time	e: 10	.30am-01.00pm Total Marks: 7	0
Instru			
	2.	Question No. 1 is compulsory. Attempt any four out of remaining six questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1		Objective Question (MCQ)	
	(a)	Choose an appropriate option from the following.	07
	1.	The frequency that has the longest period is	
		(a) 10 KHz (b) 1 KHz (c) 10 Hz (d) 1 Hz	
	2.	Ohm's law $(V = IR)$	
		(a) Can be applied to a.c similar to that of d.c.	
		(b) Can be applied to a.c. but after replacing R by Z (impedance)	
		(c) Can never be applied to a.c(d) None of the above	
	3.	The difference in period of two frequencies of 1MHz and 2 MHz is	
	J.	(a) 0.5 milli-seconds (b) 0.5 micro-seconds	
		(c) 1 milli-seconds (d) 1 micro-seconds	
	4.	Conductance is expressed in terms of	
		(a) ohm / m (b) m / ohm (c) mho / m (d) mho .	
	5.	Which resistor will be physically larger in size ?	
		(a)10 ohm, 50 W (b) 100 ohm, 10 W	
		(c) 1 kohm, 1 W (d) 10 Mohm, 1/2 W.	
	6.	The output of a logic gate is '1' when all its input are at logic 0. The gate is either	
		(a) NAND or an EX OR gate (b) NOR or an EX-NOR gate	
	7.	(c) an OR or an EX NOR gate (d) an AND or an EX-OR gate Out of following signals is an even signal.	
	7.	Out of following signals is an even signal. (a) Cosine wave (b) Sine wave	
		(c) Triangle wave (d) None of the above.	
	(b)	Choose an appropriate option from the following.	07
	1.	The circuit which magnifies a small input signal without changing its shape is	
		called an	
		(a) Linear amplifier (b) Power Amplifier	
		(c) Non-linear Amplifier (d) None of Above	
	2.	IC741 use a polarity supply.	
	2	(a) Dual (b) Single (c) Negative (d) None of Above	
	3.	Minimum bandwidth of an AM wave is	
	4.	(a) f_m (b) $2f_m$ (c) $0.5f_m$ (d) $4f_m$ PCM is aPulse Modulation Technique.	
	7.	(a) Analog (b) Digital (c) Hybrid (d) None of Above	
	5.	The first cellular systems were	
	- •	(a) Analog (b) Digital (c) Hybrid (d) None of Above	
	6.	A feedback control system is also called a	
		(a) Recursive system (b) Linear System.	
		(c) Open loop system (d) Closed loop system.	
	7.	CPU communicates with the outside world through the	
		(a) Memory (b) I/O devices (c) ALU (d) None of Above	

Q.2 (a) Define The following Terms.

(a) Interference (b) Mutual Inductance (c) Noise Margin

03

		2V + Vx - 4 \$ 6 \$ 7 \$ 8	
Q.3	(a) (b)	Draw circuit diagram of non-inverting operational amplifier & explain in brief. Explain DELTA-WYE transformation in brief with necessary equations and circuit diagrams.	03 04
	(c)	Describe low pass active filter using Operational amplifier with necessary diagrams and equations.	07
Q.4	(a) (b) (c)	What is difference between in Microprocessor and Microcontroller? What do you understand about multiplexing? Explain any one of the Multiplexing technique. Draw & Explain the functional description of digital communication system in brief.	03 04 07
Q.5	(a) (b) (c)	Reduce the given function using K-map, $F = \Sigma m(1,3,5,9,11,13)$ Write Short note on D flip flop with circuit diagram and truth table. Classify the types of Computer network? Explain each one of them in brief.	03 04 07
Q.6	(a) (b) (c)	What do you understand about isotropic radiator? Classify the standard based on 2G & 3G. What do you understand about frequency reuse concept & Why it is used in cellular system?	03 04 07
Q.7	(a) (b) (c)	Classify the Control systems. Compare Open loop and Close loop System. Compare DSB-FC, DSB-SC, SSB, VSB.	03 04 07

(c) Find the voltage Vx using superposition theorem. All resistor values are in ohm.

04

07

(b) Write a short note on Cathode Ray Oscilloscope.
